

Total No. of Printed Pages: 02

SUBJECT CODE NO:- B-2121
FACULTY OF SCIENCE & TECHNOLOGY
B.Sc. F. Y. (Sem-II)
Examination November/December- 2022
Electronics Paper-V
Digital Electronics-II

[Time: 1:30 Hours]

[Max. Marks:50]

N.B “Please check whether you have got the right question paper”

- 1) Attempt all questions.
- 2) Illustrate your answers with proper diagram.

Q.1 Describe the operation of S-R.FF Using suitable logic diagram. Give its truth. Table & symbol. 20

OR

What is Asynchronous Counter? Explain the working do of 4 bit. Asynchronous counter with. Suitable logic diagram. 20

Q.2 With neat logic diagram. Explain the working of Parallel in-Parallel out Shift Register 20

OR

Write Short notes on (any four) 20

- a) Ring counter
- b) Random asses Memory
- c) R-2R ladder type D/A Converter
- d) bidirectional shift registers
- e) DAC Characteristics.

Q.3 Attempt the following MCQ with correct answer. 10

- 1) Most basic form of flip flop may be formed by inter connecting two -----
 a) AND b) NAND c) OR d) NOT
- 2) R-S Flip Flop has active input as-----
 a) Low b) Low or high c) High d) None of above
- 3) -----Flip-flops are required for a Mod 32 Counter
 a) 64 b) 5 c)32 d)6
- 4) If a 4-bit Shift resistor is to be made using D-Filip-Flops then ----- Flip Flop are required.
 a) 2 b) 4 c) 3 d) 5
- 5) The Memory in which data stared is lost When power is turned off is ----- Memory.
 a) volatile b) permanent c) Non-volatile d) all of the above

- 6) A register is a digital ckt. with two basic function data storage &-----
 - a) clear
 - b) shifting
 - c) Movement
 - d) all a, b & c

- 7) -----flip-flops required for Mod 12 Counters
 - a) 3
 - b) 4
 - c) 12
 - d) 6

- 8) Dual slop convertor is-----
 - a) A.C. Converter
 - b) D.C. Converter
 - c) AC/DC Converter
 - d) D/A Converter

- 9) Which of the following is an example of a counter with a truncated modulus.
 - a) 8
 - b) 15
 - c) 16
 - d) 32

- 10) A shift register is a logic circuit which is -----
 - a) Sequential logic ckt.
 - b) Combinational & sequential logic ckt.
 - c) Combinational logic ckt.
 - d) None of the above