

Total No. of Printed Pages:2

SUBJECT CODE NO:- 2120
FACULTY OF SCIENCE AND TECHNOLOGY
B.Sc. F.Y Sem-II
Examination March/April-2022 (To be held in June/July-2022)
Electronics Paper-IV
Amplifiers

[Time: 1:53 Hours]

[Max. Marks:50]

Please check whether you have got the right question paper.

- N.B
- 1) Attempt all questions.
 - 2) Illustrate your answer with suitable diagram

Q.1 With neat circuit diagram. Explain the working of base bias or self bias circuit and hence derive the expressions for I_{CQ} & V_{CCQ} draw D.C load line 20

OR

Draw a neat circuit diagram of direct coupled amplifier & explain its working 20

Q.2 Explain how feedback affects the output impedance when 20

- 1) Feedback work in shunt with output
- 2) Feedback works in series with output

OR

Write short notes on the following any four 20

- a) Load line of transistor
- b) Two port network
- c) Feedback principle
- d) Band width
- e) Frequency response
- f) Decibel gain

Q.3 Attempt following MCQ with correct answer 10

1. The α for transistor is

a) $\frac{I_B}{I_E}$

b) $\frac{I_B}{I_C}$

- c) $\frac{I_C}{I_E}$ d) $\frac{I_E}{I_C}$
2. Voltage gain A_θ is the ratio of
- a) θ_i/θ_o b) $\frac{\theta_i}{I_C}$
- c) $\frac{\theta_o}{\theta_i}$ d) $\frac{\theta_o}{I_o}$
3. If the absolute power gain of an amp. Is 100 then its decibel gain is-----
- a) 40dB b) 100dB
- c) 60dB d) 20dB
4. The β for the transistor is
- a) $\frac{I_E}{I_C}$ b) $\frac{I_C}{I_E}$
- c) $\frac{I_B}{I_C}$ d) $\frac{I_C}{I_B}$
5. The gain of the amplifier after feedback -----
- a) Increases b) Decreases
- c) Remains constant d) None Above
6. Hybrid parameter means
- a) Resistance parameter b) Admittance parameter
- c) Mixed parameters d) Voltage parameters
7. Single battery operation are possible in ----amplifier.
- a) C.B. b) C.E.
- c) C.C. d) C.S
8. If the operating point changes shape of the output signal is known as -----
- a) Faithfull b) Un-faithful
- c) Thermal runaway d) Stabilization
9. In any mode the working of transistor is -in -bias
- a) Forward-reverse b) Forward- forward
- c) Releasers - forward d) Reverse-reverse
10. In common collector amplifier the voltage gains -----
- a) 1 b) gm.RL
- c) -gm.RL d) None