

Total No. of Printed Pages:1

SUBJECT CODE NO:- B-2038
FACULTY OF SCIENCE AND TECHNOLOGY
B.Sc. F.Y. (Sem-I) Examination Oct/Nov 2019
Computer Science Paper-II CS02
Digital Electronics

[Time: 1:30 Hours]

[Max. Marks: 50]

Please check whether you have got the right question paper.

N.B

- 1) Attempt all questions.
- 2) Illustrate your answer with suitable diagram.

- Q.1 a) What is gate? Explain AND & NAND gates with logical symbol. 10
 b) Explain full subtractor with suitable diagram. 10
 OR
 c) What is k-map? Explain k-map for 4 variables. 10
 d) Explain multiplexer with suitable diagram. 10
- Q.2 a) Explain D & T-flip-flops with logical symbol. 10
 b) Explain Asynchronous counter with suitable diagram. 10
 OR
 c) Write short notes on any four of the following. Each carry 5 marks. 20
 1) Hexadecimal number system
 2) Binary parallel Adder
 3) JK flip-flop
 4) Parallel-in Parallel-out shift register
 5) Demultiplexer
 6) Ring counter
- Q.3 Fill in the blank. 10
 1) $(1000)_2 = (\text{-----})_{10}$
 2) $(BC)_{16} = (\text{-----})_2$
 3) $A \cdot B + A \cdot C = A \cdot (B + C)$ is called law of -----
 4) $A \cdot \bar{A} = 0$ & $A + \bar{A} = 1$ are called laws of -----
 5) $(110100)_2 = (\text{-----})_8$
 6) $\begin{matrix} A \\ \text{---} \\ \text{---} \\ B \end{matrix} \text{---} \text{---} \text{---} \gamma$ is logical symbol of ----- gate?
 7) $(12)_{10} = (\text{-----})_2$
 8) $(1001)_2 + (1010)_2 = (\text{-----})_2$
 9) 2's complement of $(1011)_2$ is -----
 10) In two input Ex-OR gate if both input is '1' then output is -----