

Total No. of Printed Pages:2

SUBJECT CODE NO:- B-2071
FACULTY OF SCIENCE AND TECHNOLOGY
B.Sc. S.Y. (Sem-III) Examination Oct/Nov 2019
Electronics Paper-VII
Linear Integrated Circuits

[Time: 1.30 Hours]

[Max.Marks:50]

Please check whether you have got the right question paper.

- N.B
- 1) Attempt all questions
 - 2) Illustrate your answer with suitable labeled diagram.
- Q.1 Draw a neat circuit diagram of difference amplifier having dual input and difference mode output. Explain its working to determine no signal value of collector current I_{CQ} and collector to emitter voltage V_{CEQ} . 20
- OR
- Explain with circuit diagram and necessary waveforms how time IC555 is used in astable multivibrator mode.
- Q.2 Draw a neat circuit diagram of voltage shunt feedback amplifier using OP Amp and derive the expression for gain with feedback. 20
- OR
- Write short notes on any four of the following
- a) Characteristics of an ideal OP Amp
 - b) OP Amp differentiator
 - c) Timer IC555 as frequency divider
 - d) OP Amp comparator
 - e) Phase shift oscillator
 - f) OP Amp as dc low voltage dc voltmeter
- Q.3 Attempt the following multiple choice questions 10
- 1) Cascade difference amplifier requires level translator because
 - a) Impedance matching
 - b) Isolation of each stage
 - c) dc shift
 - d) ac shift
 - 2) What is the scale of multiplier of an integrator
 - a) R/C
 - b) C/R
 - c) -RC
 - d) -1/RC
 - 3) What is Pin - 7 of timer IC555
 - a) Trigger
 - b) Threshold
 - c) Discharge
 - d) Reset
 - 4) What controls the output pulse width of a monostable multivibrator
 - a) The external clock frequency
 - b) The width of clock pulse
 - c) RL time constant
 - d) RC time constant

- 5) An oscillator requires
- a) + ve feedback b) -ve feedback
c) No feedback d) Both +ve & -ve feedback
- 6) Condition for sustaintion of weinbridge oscillator is
- a) $(1 + Rf/R) = 3$ b) $(1 + Rf/R) = \infty$
c) $(1 + Rf/R) = 6$ d) $(1 + Rf/R) = 29$
- 7) A current to voltage converter produces
- a) A constant output voltage for a variable input current
b) Variable output voltage for a constant input current
c) Proportional output voltage for a variable input current
d) Proportional output current for a variable input current
- 8) If V_1 and V_2 are two input voltages of an ideal OPamp then output voltage V_o is
- a) $V_1 - V_2$ b) $A \times (V_1 - V_2)$ c) $A \times (V_1 + V_2)$ d) $V_1 \times V_2$
- 9) What is the output voltage of inverting summing amplifier if
- $R_1 = R_2 = R_3 = 100\Omega, R_f = 1 K \Omega$
 $V_1 = V_2 = V_3 = 10mv$
- a) 0.3 V b) -0.3V c) 3V d) -3V
- 10) In an LC oscillator the frequency of oscillations is ----- L or C
- a) Proportional to square root of b) Inversely proportional to square root of
c) Proportional to square of d) Directly proportional