

Total No. of Printed Pages: 3

**SUBJECT CODE NO: - Y-2171**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**B.Sc. (PATTERN-2013) (S.Y SEM IV)**  
**Examination April / May - 2024**  
**Physics Paper-XI (General Electronics)**

[Time:1:30 Hours]

[Max. Marks:50]

Please check whether you have got the right question paper.

N. B

- 1) Attempt all questions.
- 2) Use of Logarithmic table and calculator is allowed.

**Q.1** a) Explain with neat circuit diagram, input and output characteristics of common base configuration of transistor. **10**

b) What is op- Amp? Explain how Op-Amp works as a subtractor. **10**

**OR**

a) What is phase shifting network? With neat circuit diagram, explain the working of phase shift oscillator. **10**


b) What is phase modulation? Derive an expression for phase modulated wave. **10**

**Q.2** a) Distinguish between Bipolar junction transistor (BJT) and Field effect transistor (FET). **5**

b) For an N-channel JFET,  $I_{DSS} = 8.2\text{mA}$ , and  $V_p = -3\text{V}$  And  $V_{GS} = -1\text{V}$ . Find the Value of  $I_D$ . **5**

c) What is feedback? Explain positive feedback. **5**

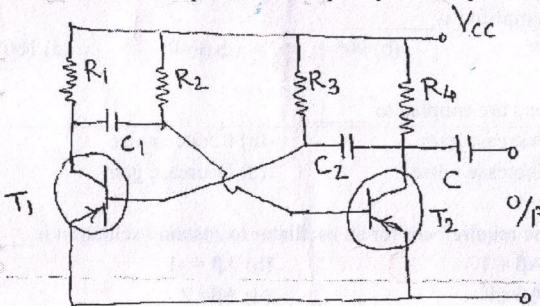d) In the astable multivibrator,  $R_2 = R_3 = 10\text{ k}\Omega$  and  $C_1 = C_2 = 0.01\text{ }\mu\text{f}$ . Determine the time period and frequency of the square wave. **5**



OR

- a) Discuss merits and demerits of RC coupled amplifier. 5
- b) A transistor uses potential divider method of biasing. calculate the collector current if voltage across  $R_2=4Y$ ,  $V_{BE} = 0.7V$  and  $R_E = 2K\Omega$ , 5
- c) What are the limitations of amplitude modulation? 5
- d) A sinusoidal carrier voltage of frequency 1 MHz and amplitude 200 V is amplitude modulated by sinusoidal Voltage of frequency of 4 kHz producing 40% modulation, calculate the frequency and amplitude of lower and upper sideband terms. 5

## Q.3 Multiple choice questions.

10

- 1) A zener diode should have \_\_\_\_\_  
 (a) Narrow depletion region (b) Lightly doped p and n region  
 (c) Heavily doped p and n region (d) Both a and c.
- 2) As the temperature of a transistor goes up, the base-emitter resistance \_\_\_\_\_  
 (a) Increases (b) Decreases  
 (c) Remains constant. (d) None of these
- 3) A MOSFET is sometimes called as \_\_\_\_\_ JFET.  
 (a) Open gate (b) Short gate  
 (c) Insulated gate (d) None of these.
- 4) The value of stability factor for a base resistor bias method is \_\_\_\_\_  
 (a)  $(1-\beta)$  (b)  $(1+\beta) R_B$   
 (c)  $(1+\beta)$  (d)  $(1+\beta) R_c$
- 5) The phase difference between the output and input voltage of a common emitter amplifier is \_\_\_\_\_  
 (a)  $0^\circ$  (b)  $90^\circ$  (c)  $360^\circ$  (d)  $180^\circ$
- 6) Amplifiers are coupled to \_\_\_\_\_  
 (a) Increase gain (b) Reduce noise  
 (c) Increase noise (d) Decrease gain
- 7) The basic requirement for an oscillator to sustain oscillation is \_\_\_\_\_  
 (a)  $A\beta = 1$  (b)  $A\beta = -1$   
 (c)  $A\beta = 0$  (d)  $A\beta = 2$



- 8) In the Hartly oscillator circuit if  $L_1 = 100 \mu\text{H}$ ,  $L_2 = 1 \text{ MH}$  and mutual inductance between the coils,  $M = 20 \mu\text{H}$ , then total inductance is \_\_\_\_\_
- (a)  $1140 \mu\text{H}$  (b)  $1250 \mu\text{H}$   
(c)  $1030 \mu\text{H}$  (d) None of these
- 9) In amplitude modulated wave equation, the sum of carrier frequency and signal frequency is called \_\_\_\_\_
- (a) Lower side band frequency.  
(b) Upper side band frequency  
(c) Carrier frequency,  
(d) None of these.
- 10) Demodulation is done in \_\_\_\_\_
- (a) Receiving antenna (b) Transmitting antenna  
(c) Transmitter (d) Radio receiver.

